



MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE

By

Kirby Creel,
Engineering Manager,
Datatronics

This article is a general discussion of distributed capacitance, C_d , in transformers with emphasis on measurement. We will discuss how capacitance occurs, references to formula for calculating, how capacitance is modeled, how C_d is measured (with three cautionary notes) and guidelines to aid in evaluating / measuring C_d .

Capacitance in a transformer winding cannot be avoided. The voltage difference between turns, between winding layers and between windings to core create these parasitic elements. In general, part of the designers' task is to keep capacitance to a minimum. On rare occasions winding capacitance is increased to reduce ringing in switching transformers.

There are several capacitive elements in a transformer. Capacitance occurs winding to winding, turn to turn, windings to core and stray capacitances between terminals and case. To better understand the capacitance phenomenon in transformers, see REF [1, 2 & 3]. Reference [6] is an article aimed at C_d of coils for higher frequency applications with several test methods. This discussion will be aimed at the measured capacitance that appears across a winding in a transformer. Each winding in a transformer will add capacitance to this total. Transformer action will cause the sum of reflected capacitances to appear at the terminals of each winding.

MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE

by Kirby Creel

In the literature, the capacitance appearing across the terminals of an inductor are almost universally identified as the distributed capacitance "Cd". Authors identify the parasitic capacitive elements of a transformer with various symbols. For this discussion, distributed capacitance "Cd" will be the total capacitance. The total is the winding capacitance of a winding used as the reference plus the sum of capacitances of all other windings reflected by the square of the turns ratio. See (Equation 1) below.

$$C_d = C_{(REF)} + C_{(A)} \left(\frac{N_{(a)}}{N_{(REF)}} \right)^2 + C_{(B)} \left(\frac{N_{(B)}}{N_{(REF)}} \right)^2 + \dots \quad [EQ.1]$$

To illustrate with an example, consider the transformer schematically shown in Figure 1. The example was made by testing SRF (Self Resonant Frequency) after each winding was added and the capacitance increase by each winding was calculated. Each winding has the turns and the related capacitance identified. If this transformer were to be modeled in one of the circuit analysis programs, the transformer as shown would be acceptable.

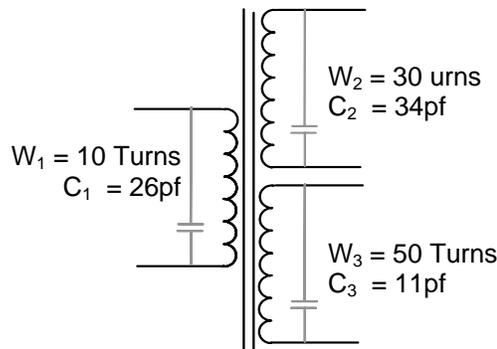


FIGURE 1

Table 1 illustrates how each capacitance reflected to a reference winding creates the Cd "total". (see EQ.1) Note that in the last column of the table, the SRF is calculated from the reference winding inductance and Cd. The transformer action causes the reflected capacitances to appear in a ratio that makes the SRF the same with different turns. The fact that all windings will have the same SRF is not intuitive. Transformers with poor coupling between windings or a strong drive sensitivity will have differences in SRF.

Reference Winding	Effective Capacitance Reflected to reference winding (pF)			Cd Total (pF)	L(mH)	SRF MHZ
	C ₁	C ₂	C ₃			
W ₁	26.00	306.00	275.00	607.00	.04	1.0214
W ₂	2.89	34.00	30.56	67.45	.36	1.0214
W ₃	1.04	12.24	11.00	24.28	1.00	1.0214

NOTE: VALUES SHOWN IN (BOLD) ARE GIVEN. ALL OTHERS ARE CALCULATED.

TABLE 1

MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE by Kirby Creel

When modeling a transformer, the capacitance can be included with one of the total values rather than the three individual values. See Figure 2.

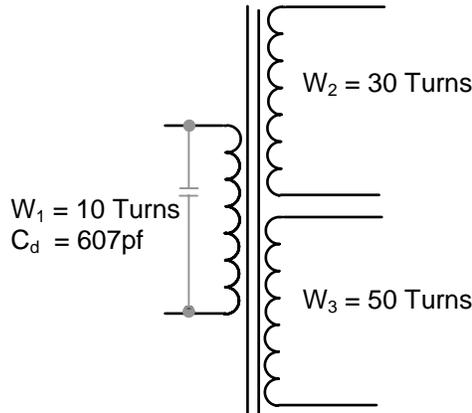


FIGURE 2

Having an accurate value for C_d is important in circuit modeling. As the frequency of operation increases the capacitance effects play a larger role in the operation of the circuit and a correct value for the model becomes more important.

The measurement of C_d is a complex operation that requires care. C_d cannot be measured directly. The "standard" method is to measure the SRF of a transformer (or inductor) and calculate the C_d , see EQ. 2.

$$C_d = \frac{\left(\frac{1}{2\pi(\text{SRF})} \right)^2}{L} \quad \begin{array}{l} \text{SRF is in Hertz} \\ \text{Inductance is in Henries} \\ \text{Cd in Farads} \end{array} \quad [\text{EQ.2}]$$

The total capacitance of the device that resonates with the inductance of the winding tested is the C_d . Experience shows that this result is considered axiomatic by many Engineers. In a majority of devices this method will provide the correct value of C_d . This article describes three factors that can cause the measured value to be in considerable error. To demonstrate each of these factors, an example is provided to give the reader a better understanding of the problem.

In each of the example coils, a toroid core was selected. Toroids most closely demonstrate the material characteristic curves provided by manufacturers. Any gap in a core structure will effect the material characteristics. In a gapped core, the following factors will still cause error in the readings but the effect will be reduced.

MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE
by Kirby Creel

1) The first error factor is caused by measuring the inductance of the device at a drive level that exaggerates the inductance at SRF. A coil was wound on an "R" material core and the inductance was tested with 1.0 volt at 1.0 kHz. (The 1 volt at 1 kHz is a typical specified value.) The same coil was tested with .01 volts at 10 kHz. Table 2 shows the calculation of the Cd based on the two measured inductance values. Most ferrite materials have inductance values that are sensitive to the drive level. In this case, Magnetics Incorporated "R" material was selected. The material permeability varies with drive level. See Figure 3 below. The possible error as shown in the curve is greater than 2:1. The solution to this factor is to measure the inductance at a low flux level. As a guideline use 10 gauss maximum.

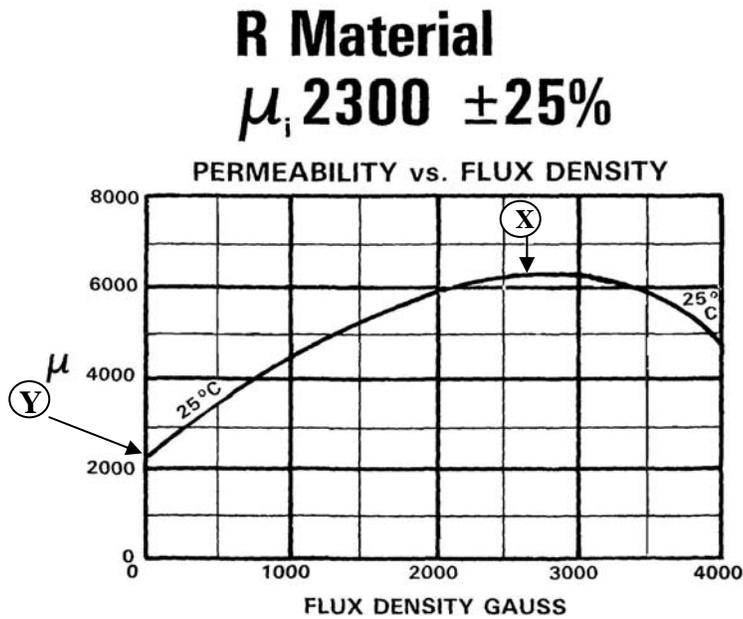


FIGURE 3 [REF. 4]

TEST VOLTAGE	INDUCTANCE	SRF	CALCULATED Cd pF
1.0V at 1.0 kHz	7.60 mH (POINT X)	703 kHz	6.74
0.01V at 10 kHz	4.16 mH (POINT Y)		12.32

TABLE 2

MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE
by Kirby Creel

- 2) The second error factor is more subtle. The error is caused by the drop in permeability as the frequency of the applied signal is increased. See Figure 4. Note that the “H” Material curve is typical of a production lot and does not constitute a guaranteed response. Experience has shown that individual lots will vary widely. A coil was wound using "H" material and the inductance tested at a low flux level at 10 kHz.

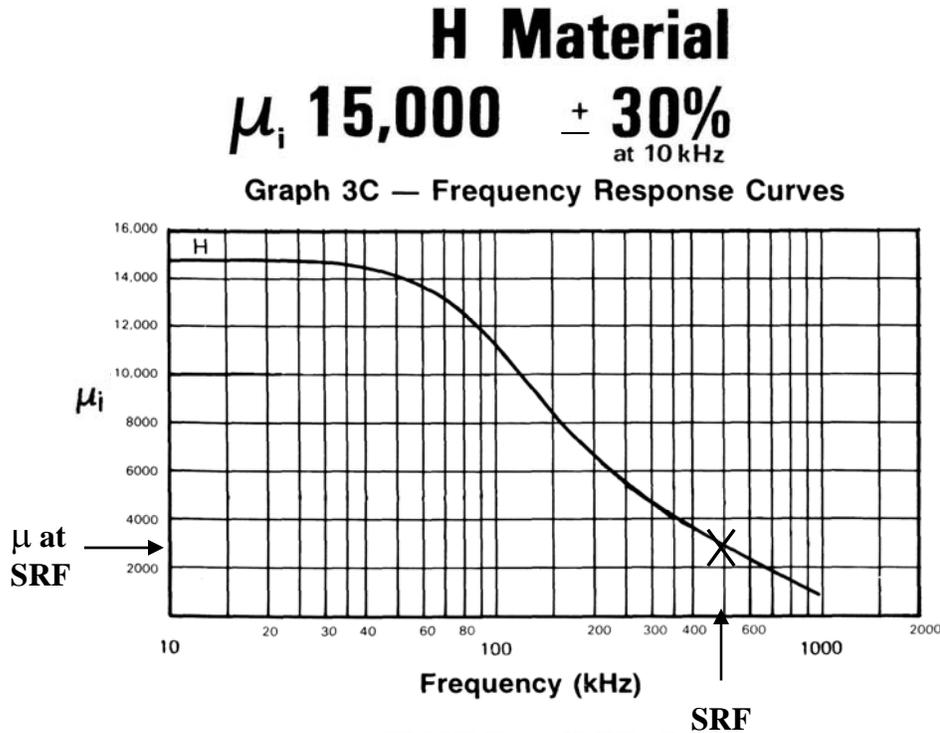


FIGURE 4 [REF. 4]


The SRF was measured and Cd calculated. The question becomes what is the "true" Cd ? The answer can be “measured” by winding an identical coil on a core that is not subject to the drop in permeability with increased frequency. A second coil was wound on a core made from Magnetics "A" material using the identical winding technique. Table 3 shows readings and calculations. The calculated error is about 46%. Figure 4 shows the possibility of errors approaching 5:1.

FERRITE MATERIAL	INDUCTANCE	SRF	CALCULATED Cd pF
H	38.5 mH	499 kHz	2.64
A	1.734 mH	1.565 MHz	5.96

TABLE 3

MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE
by Kirby Creel

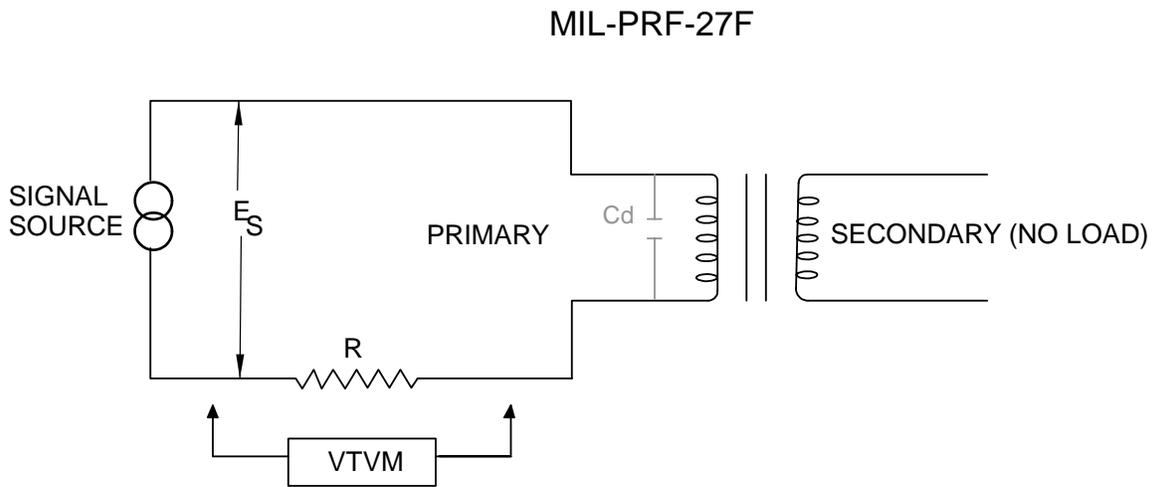3) The third error factor has to do with the SRF measurement method. The generally accepted method is to find the maximum impedance point of the device. The impedance of a parallel resonant circuit reaches a maximum at the resonant frequency. By measuring the "line" current using the voltage across a series element the maximum impedance point can be determined. One source of the test method is shown in Figure 5 from military specification MIL-PRF-27. Paragraph 4.7.12.9 of the Military Specification defines the SRF as the frequency that the minimum dip in voltage occurs on the VTVM. The definition of SRF is the frequency at which the distributed capacitance resonances with the self inductance and the reactive components cancel. The maximum impedance point and the SRF can be quite different.



Measurement of SRF
FIGURE 5.

MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE
by Kirby Creel

Figure 6 shows the phase angle of current plotted against frequency, using a Hewlett Packard HP-4194A. The plot is the same coil as discussed in (2). The resonant frequency is 499 KHz (zero in this case is actually $+0.00084^\circ$). Figure 7 is the exact same display with the impedance included. The impedance maximum occurs at 703 KHz. The point where the phase angle is zero (resonance) does not coincide with the maximum impedance point.

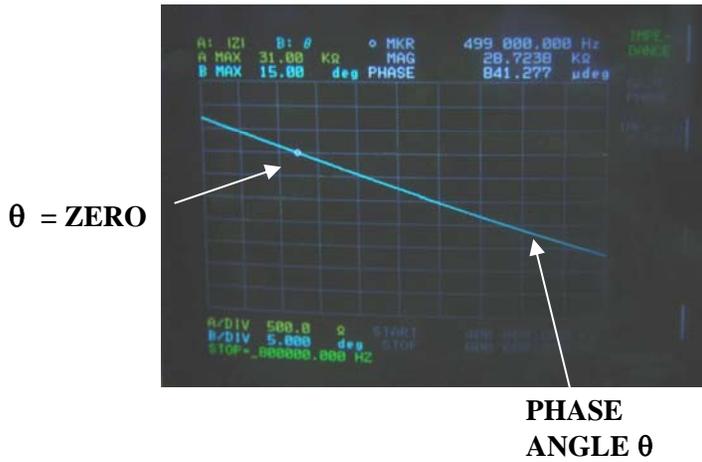


FIGURE 6

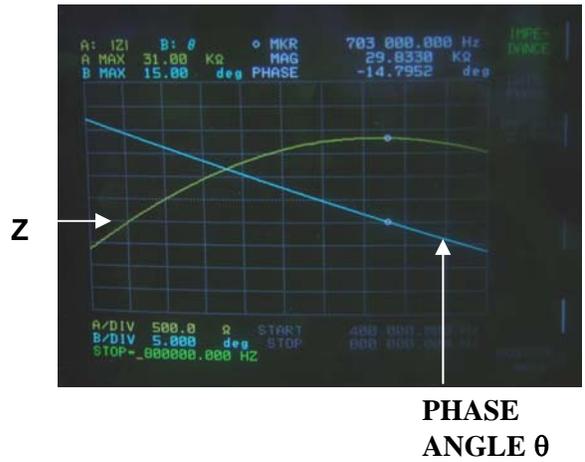


FIGURE 7

The Cd is calculated in table 4. Results of the “A” material from Table 3 are included. Note the large difference in the calculated values. Selection of the test method (SRF or maximum “Z”) may give very different results.

FERRITE MATERIAL	INDUCTANCE	SRF $\theta = 0$	MAX “Z”	CALCULATED Cd (pF)
H	38.5 mH	---	703 KHz	1.33
H	38.5 mH	499 KHz	---	2.64
A	1.734 mH	1.565 MHz	1.565 MHz	5.96

TABLE 4

MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE

by Kirby Creel

All three of the errors noted will give Cd values lower than the actual. In a worst case scenario, the total error may be greater than a factor of 10. Below are some guidelines to help the reader to anticipate when to expect errors and how to avoid them in determining Cd.

Problem indicators

- a) High permeability cores (includes nickel laminations)
- b) Toroid cores (includes nickel strip)
- c) Ferrite cores
- d) High perm MPP
- e) Cores that are permeability sensitive with level or frequency
- f) High turns ratios (error effects are multiplied)
- g) Applications where the Cd is a critical parameter

Indicators of fewer problems

- h) Low perm cores
- i) Gapped core structure
- j) Bobbin style windings (measurements can be made on the wound bobbin before core is installed)

Measurement guidelines

- k) Take inductance measurement at a low level
- l) Review the core characteristics to anticipate whether frequency or test level will effect the readings.
- m) Determine the measurement method (impedance or frequency)
- n) Calculate a predicted value. Reconcile any significant difference.
- o) Wind / test another core that is not as sensitive to level or frequency.
- p) Because the results may be in pF, extra care must be exercised in zeroing out errors in fixtures or test leads.
- q) If the individual capacitances are of interest, test SRF after each winding. The capacitance added by each winding can be calculated.
- r) The following ESTIMATED Cd for toroids with a single winding is provided as a "sanity" check. See REF [5] . For more than one winding, (all windings with a ratio of 1:1) multiply the estimated capacitance by the number of windings -
 - Small (less than .25" OD) = 6 to 10 pF
 - Medium (.25" to 1" OD) = 10 to 25 pF
 - Large (greater than 1" OD) = 25 to 75 pF

The author thanks Magnetics Incorporated for their help in supplying sample cores and allowing the reprint of their material characteristic curves.

MEASURING TRANSFORMER DISTRIBUTED CAPACITANCE
by Kirby Creel

REFERENCES

- 1) Snelling, E.C., 1988.
Soft Ferrites, 2nd Edition, Butterworth and Co. Ltd.
ISBN 0-408-02760-6
Chapter 11
- 2) Lee, Wilson and Carter, 1988.
Electronic Transformers and Circuits, 3rd Edition, John Wiley and Sons
ISBN 0-471-81966-X
Chapter 5.9
- 3) Grossner, Nathan R., 1983.
Transformers for Electronic Circuits, 2nd Edition, Mc Graw-Hill Book Company
ISBN 0-07-024979-2
Chapter 9.4
- 4) Magnetics – Division of Spang and Company
Ferrite Cores (Catalog)
FC-601, 2003
- 5) Magnetics – Division of Spang and Company
Powder Cores MPP and High Flux Cores (Catalog)
MPP-303X-1Y, 1991
“Distributed capacitance”, Page 10
- 6) Tawney, Gereld L.
Inductors: Their Self Resonance and Distributed Capacitance,
Powerconversion International, vol. 8, no. 4, April 1982, ISSN 0199-1884

The only sources of reference (6) found were the Linda Hall Library in Kansas City, Missouri, “lhl.lib.mo.us” or Canada Institute for Scientific and Technical Information (CISTI) “cat.cisti.nrc.ca”